

# Electrical Engineering Technology

---

**ECET 17700 - DAQ & Control Systems**

*Lecture # 9 – Loading, Thévenin & Norton*


Professors Robert Herrick & J. Michael Jacob

## Module 4


# Source Conversion

# Lecture 9 Modules


---

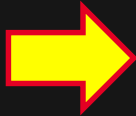1. Circuit Loading
2. Thévenin Circuit Model – *What's in the Box*
3. Norton Circuit Model
-  4. **Model Conversion**
5. What's in the Box – Practical Measurements
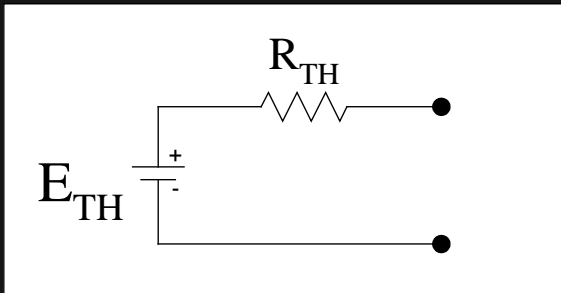
# Equivalent Models - *supply conversion*



*Thévenin model*

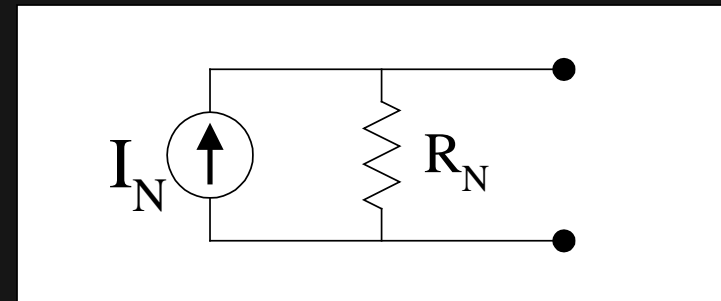


*Norton model*


**Same load  
results !**

# $R_{TH}$ & $R_N$ - *supply conversion*

4

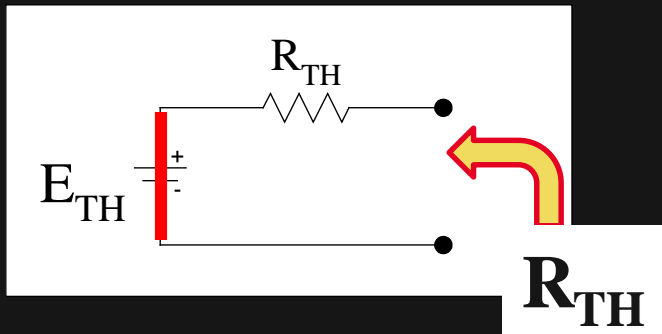

*Thevenin model*

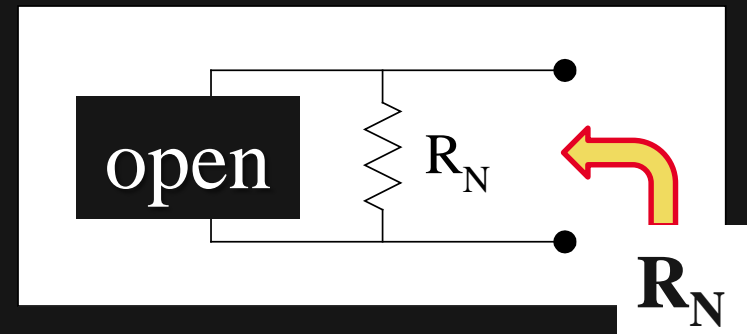


*Norton model*

Zero the sources


$$R_{TH} = R_N$$



# $I_N$ - *supply conversion*

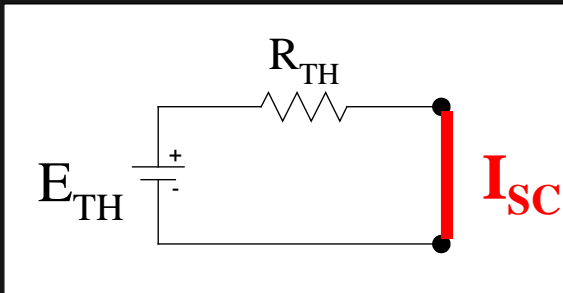

*Thevenin model*

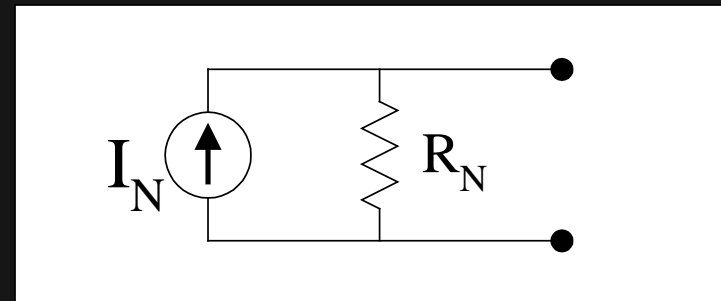


*Norton model*

*Short Circuit Current*


$$I_N = E_{TH} / R_{TH}$$


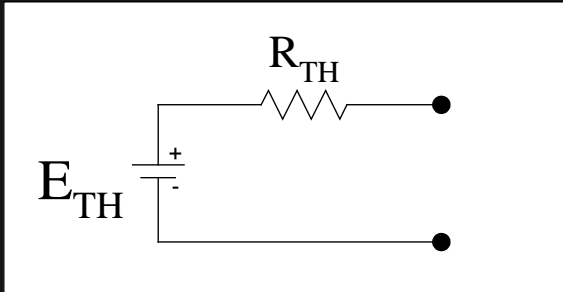
# $E_{TH}$ - *supply conversion* <sup>6</sup>



**Thevenin model**

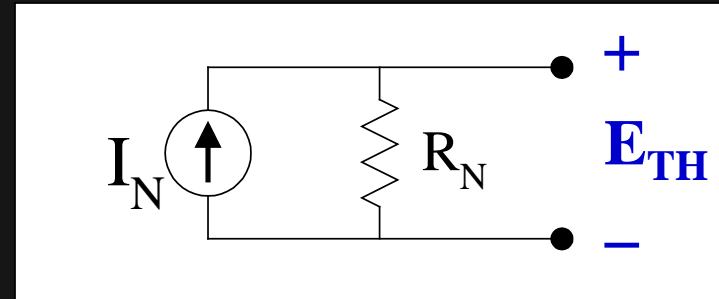

***Norton model***

Open Circuit Voltage



$$E_{TH} = I_N \times R_N$$

# Thevenin Resistance

---




$$R_{TH} = R_N = V_{OC} / I_{SC}$$



*Warning - SHORT can cause smoke or loading !*
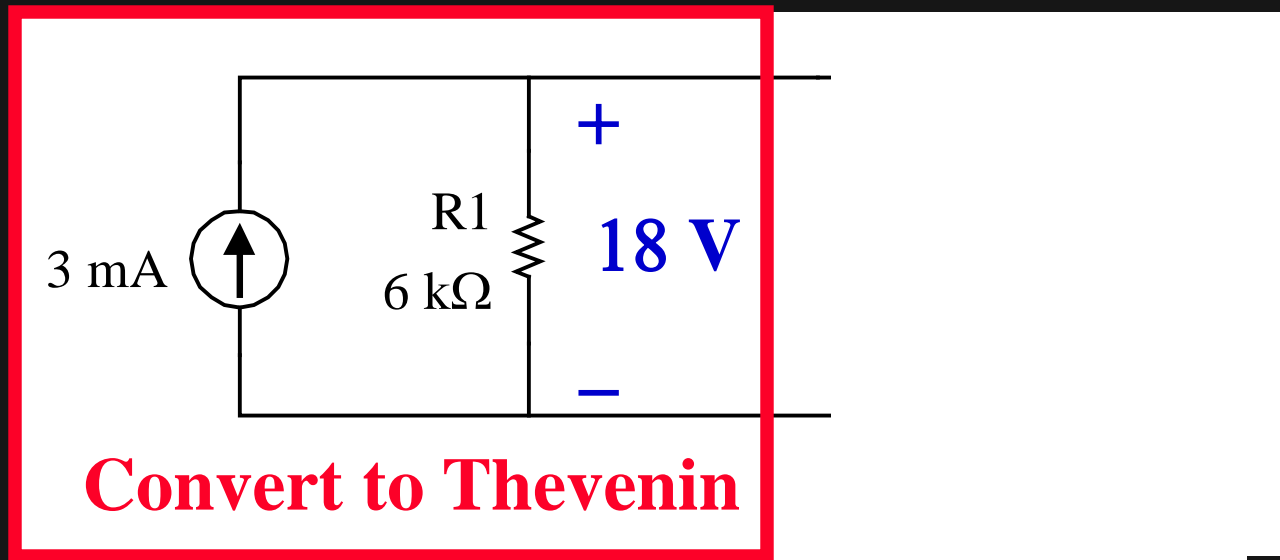
# Equivalent Circuit - *source conversion*




$$R_{TH} = R_N = 6 \text{ k}\Omega$$

$$E_{TH} = 3\text{mA} \times 6 \text{ k}\Omega = 18\text{V}$$



# Example model - *source conversion*

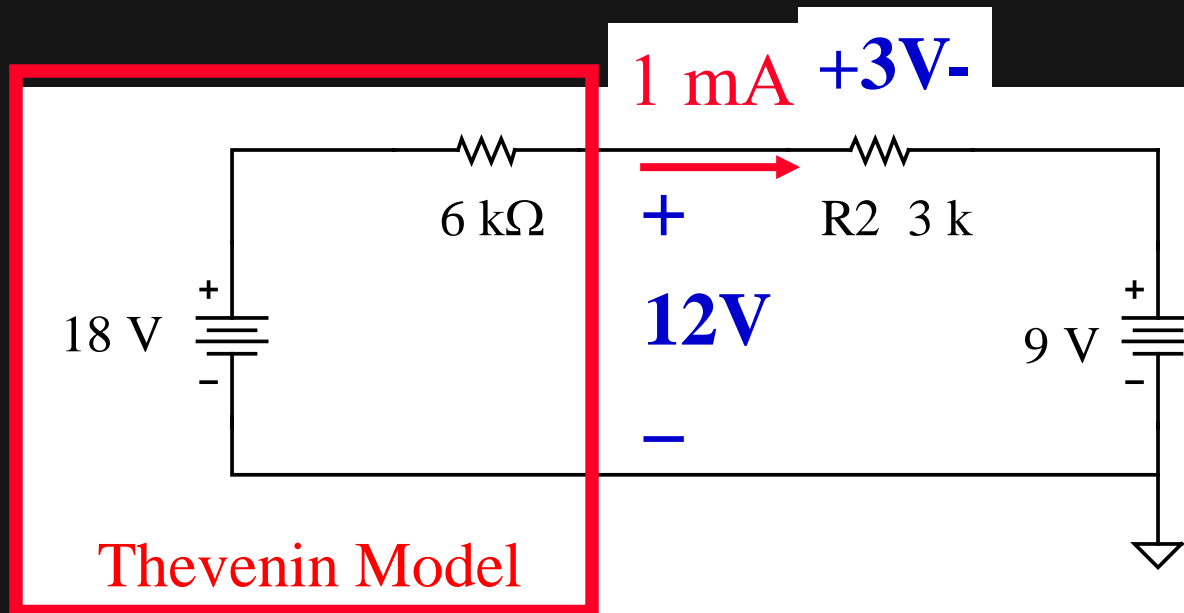


$$E_{\text{NET}} = 18\text{V} - 9\text{V} = 9\text{V}$$

$$R_{\text{T}} = 6\text{ k}\Omega + 3\text{ k}\Omega = 9\text{ k}\Omega$$

$$I_{\text{R2}} = 9\text{V} / 9\text{k}\Omega = 1\text{ mA}$$

# Switch Back to Original Circuit

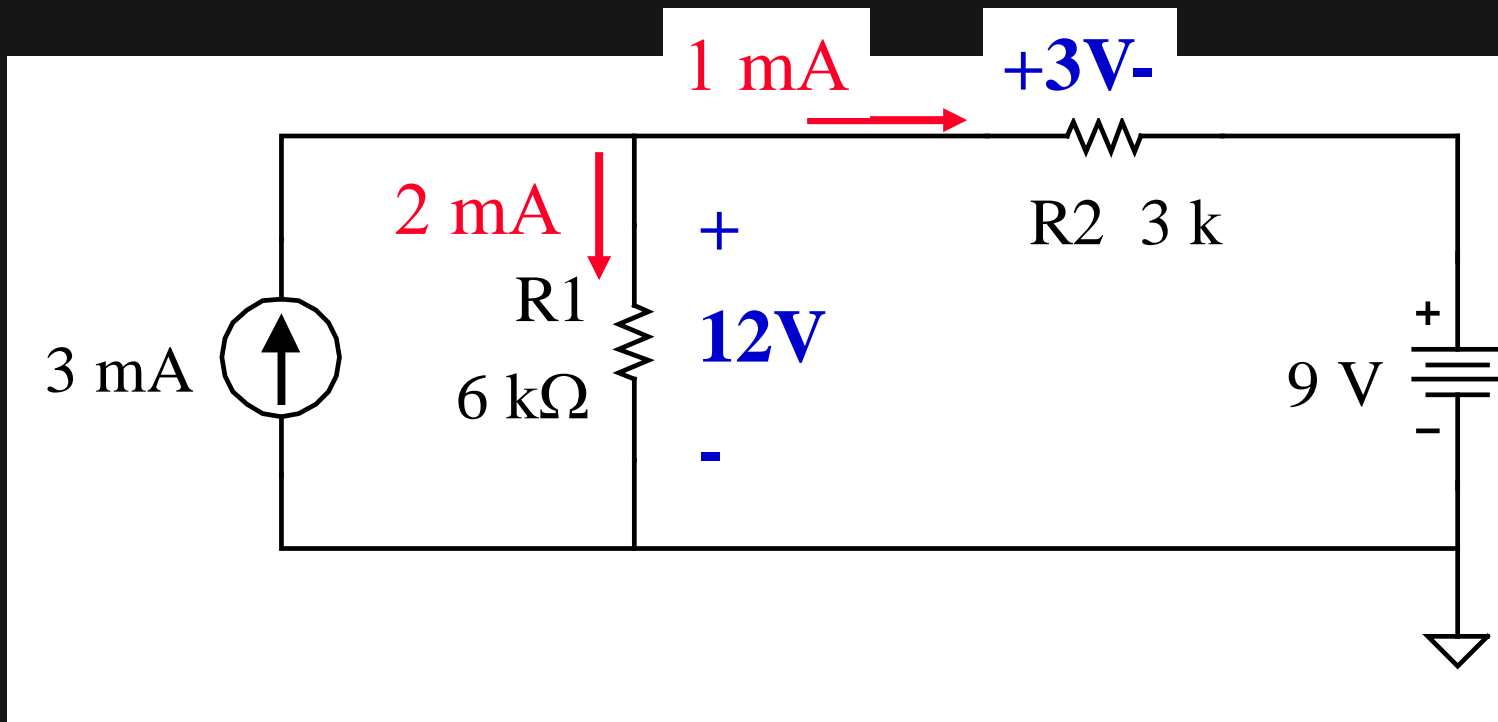


$$I_{R1} = 3 \text{ mA} - 1 \text{ mA} = 2 \text{ mA}$$

$$V_{R1} = V_{I\text{supply}} = 2 \text{ mA} \times 6 \text{ k}\Omega = 12 \text{ V}$$

# Lecture 9 Modules

---

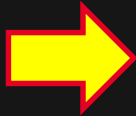1. Circuit Loading
2. Thévenin Circuit Model – *What's in the Box*
3. Norton Circuit Model
-  4. **Model Conversion**
5. *What's in the Box* – Practical Measurements